

12 Cálculo Szi $\times_{c} + Z_{o}$ \circ (6) \rightarrow (11): $b_2 = V_2 - I_2 Z_0$ (11) Xc + Zo b2 = V, Zo + V, Zo $\frac{\times_{c} + Z_{o}}{2\sqrt{Z_{o}}} \times \frac{\times_{c} + Z_{o}}{\times_{c} + Z_{o}} = \frac{2\sqrt{Z_{o}}}{\times_{c} + Z_{o}} \times \frac{2\sqrt{Z_{o}}}{\times_{c} + Z_{o}} = \frac{2\sqrt{Z_{o}}}{\sqrt{Z_{o}}} \times \frac{2\sqrt{Z_{o}}}{\sqrt{Z_{o}$ ×c+Z0 = 2√Z0 $\cdot (15), (8) \rightarrow (2)$ $\sqrt{\frac{20/x_{c}+z_{o}}{\sqrt{20}}}$ $\sqrt{\frac{9z_{o}/x_{c}+z_{o}}{\sqrt{20}}}$ $\sqrt{\frac{9z_{o}/x_{c}+z_{o}}{\sqrt{20}}}$ $\sqrt{\frac{1+z_{o}/x_{c}+z_{o}}{\sqrt{20}}}$ $S_{21} = 2Z(0).Z = Z_0$ 1+Z $\times_{c}+Z_{0}$ 4 Por simétros e reciprocidade, temos que: S22 = S11 e S12 = S21 La Para f=1GHz, C=1pFe=Zo=501, temos: $X_{c} = 1$ = 1 $\Rightarrow X_{c} = -j159,15$ $j2\pi f.c$ $j2\pi.1 \times 10^{9}.1 \times 10^{-12}$

$$7 - \frac{1}{20} = \frac{50}{159,15} = \frac{50}{166,82/-72,56}$$

$$S_{11} = 1 - (0.09 + j.0.286) = 0.91 - j.0.286 = 0.954 / -17.45$$

 $1 + (0.09 + j.0.286) = 1.09 + j.0.286 = 1.127 / 14.70°$

$$S_{21} = \frac{0.6/72,56^{\circ}}{1,127/14,70} = 0.532/57,86^{\circ} = S_{12}$$

· Provo Real:

La No Livro "Microwave and RFDesign network, Volume 3 de Michael Steer, temos para uma conexão em serie: $S_{11} = S_{22} = \overline{Z}$; $\overline{Z} = \overline{Z}/\overline{Z}_0$ $\overline{Z} + 2$

$$S_{21} = S_{12} = \frac{2}{7}$$

$$Z = -5159715 = 159715 / -90^{\circ} = 3183 / -90^{\circ} = 0 - 3183$$

in a second contract of	S11 = 3, 183/-90 = 3, 183/-90 = 0, 847/-32, 19°
	2-53,183 3,759/-57,86
	$S_{21} = 2$ = 0,532/57,86°
	3,759/-57,86°
	La Assim comprovanda os valores encontrados
- 1-	E 1 6 2 2 2 2 2 2 2 2 2 2 2 2 2 2 2 2 2 2
	12 - 136 - O (- 10) (C (- 1)) (O (- 1)